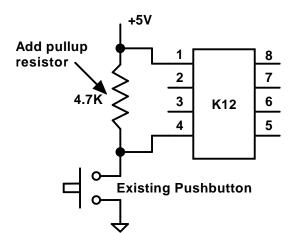
The K12 requires a pullup on pin 3, the pushbutton input.



Simply solder a 4.7K 1/4 or 1/16 watt resistor between ppin pads 1 and 4 on the bottom (solder) side of the PC board.

